

Architetture e reti logiche

Esercitazioni VHDL

a.a. 2005/06


Componenti sequenziali in VHDL

Stefano Ferrari



Università degli Studi di Milano
Dipartimento di Tecnologie
dell'Informazione

Flip-flop di tipo D

 

d	clk	q
0	↑	0
1	↑	1
—	—	q

```
entity FF_D is  
  port (d, clk: in bit;  
         q: out bit);  
end FF_D;
```


Flip-flop D: modello comportamentale

```
architecture behav1 of FF_D is
begin
  process (clk)
  begin
    if (clk'event and clk='1') then
      q <= d;
    end if;
  end process;
end behav1;
```

Flip-flop D: modello comportamentale (2)


```
architecture behav2 of FF_D is
begin
  process -- no sensitivity list
  begin
    wait until clk'event and clk='1';
    q <= d;
  end process;
end behav2;
```

Registro a n bit

 

```
entity REG4 is
  port ( d: in bit_vector(0 to 3);
         clk: in bit;
         q: out bit_vector(0 to 3))
end REG4;
```

Registro a 4 bit: modello strutturale

 


Registro a 4 bit: modello strutturale (2)

```

architecture STRUCT of REG4 is
  component FF_D
    port (d, clk: in bit;
          q: out bit);
  end component;
begin
  u1: FF_D port map (d(0), clk, q(0));
  u2: FF_D port map (d(1), clk, q(1));
  u3: FF_D port map (d(2), clk, q(2));
  u4: FF_D port map (d(3), clk, q(3));
end STRUCT;

```

Flip-flop di tipo SR

 

<i>s</i>	<i>r</i>	<i>clk</i>	<i>q</i>
0	0	↑	<i>q</i>
0	1	↑	0
1	0	↑	1
1	1	↑	X
-	-	0	<i>q</i>
-	-	1	<i>q</i>

```

entity FF_set_reset is
  port (s, r, clk: in std_logic;
        q: out std_logic);
end FF_set_reset;

```

Flip-flop SR: modello comportamentale

```

architecture BEHAV of FF_set_reset is
begin
  process (clk)
  begin
    if (clk'event and clk='1') then
      if (s='1' and r='1') then
        q <= 'X';
      elsif (r='1') then
        q <= '0';
      elsif (s='1') then
        q <= '1';
      end if;
    end if;
  end process;

```


Flip-flop SR con reset asincrono

```

architecture BEHAV2 of FF_set_reset is
begin
  process (clk, r)
  begin
    if (r='1') then -- reset asincrono e prioritario
      q <= '0';
    elsif (clk'event and clk='1') then
      if (s='1') then
        q <= '1';
      end if;
    end if;
  end process;
end BEHAV2;

```


Contatore

 

# fronti	out
0	"0000"
1	"0001"
2	"0010"
3	"0011"

Contatore a n bit \Leftrightarrow Contatore modulo 2^n

Contatore (2)

 


Contatore con reset

```


architecture behav of cont8 is
  signal t: std_logic_vector(0 to 7);
begin
  process(clk, reset)
  begin
    if (reset = '1' ) then
      t <= "00000000";
    elsif (clk'event and clk = '1' ) then
      t <= t + "00000001";
    end if;
  end process;
  outa <= t;  -- assegnamento concorrente
end behav;

```

Contatore completo

 

Shift register

 

```
entity ShiftRegister is
  port (
    d, clk : in std_logic;
    q : out std_logic);
end ShiftRegister;
```

Il numero di bit del registro non compare nell'interfaccia.

Shift register (2)

```
architecture behav of ShiftRegister is
  signal t : std_logic_vector(0 to 3);
begin
  process (clk)
  begin
    if clk'event and clk = '1' then
      t <= d & t(0 to 2);
      q <= t(3);
    end if;
  end process;
end behav;
```

Shift register: segnali addizionali

<i>reset</i>	pone tutti i bit a "0"
<i>set</i>	pone tutti i bit a "1"
<i>right/left</i>	direzione dello scorrimento
<i>enable</i>	abilita/disabilita lo scorrimento
<i>data in/load</i>	scrittura parallela
<i>data out</i>	lettura parallela