

Architetture e reti logiche

Esercitazioni VHDL

a.a. 2008/09


Componenti combinatori in VHDL

Stefano Ferrari



UNIVERSITÀ DEGLI STUDI DI MILANO
DIPARTIMENTO DI TECNOLOGIE DELL'INFORMAZIONE

Decoder a due ingressi

 

```
entity DEC24 is
  port (A, B: in bit;
        Z: out bit_vector (0 to 3));
end DEC24;
```

Decoder: descrizione dataflow

```

architecture DATA_FLOW1 of DEC24 is
begin
  Z <= "1000" when (A='0' and B='0')
        else "0100" when (A='0' and B='1')
        else "0010" when (A='1' and B='0')
        else "0001";
end DATA_FLOW1;

```


Decoder: descrizione dataflow (2)

```

architecture DATA_FLOW2 of DEC24 is
  signal t: bit_vector(0 to 1);
begin
  t <= A & B;
  with t select
    Z <= "1000" when "00", -- 0
        "0100" when "01", -- 1
        "0010" when "10", -- 2
        "0001" when "11"; -- 3
end DATA_FLOW2;

```

Decoder: rappresentazione circuitale

 

```

architecture DATA_FLOW3
  of DEC24 is
  begin
    Z(0) <= (not A and not B);
    Z(1) <= (not A and B);
    Z(2) <= (A and not B);
    Z(3) <= (A and B);
  end DATA_FLOW3;

```

Decoder: descrizione strutturale

```

architecture STRUCT of DEC24 is
  component INV
    port (A: in bit;
          Z: out bit);
  end component;
  component AND2
    port (A, B: in bit;
          Z: out bit);
  end component;
  signal NOT_A, NOT_B: bit;
begin

```

(continua)

Decoder: descrizione strutturale (2)


(continua)

```

begin
  u1: INV port map (A, NOT_A);
  u2: INV port map (B, NOT_B);
  u3: AND2 port map (NOT_A, NOT_B, Z(0));
  u4: AND2 port map (NOT_A, B, Z(1));
  u5: AND2 port map (A, NOT_B, Z(2));
  u6: AND2 port map (A, B, Z(3));
end STRUCT;

```

Multiplexer a due vie

 

SEL	A	B	Z
0	0	—	0
0	1	—	1
1	—	0	0
1	—	1	1

```

entity MUX2 is
  port (A, B, SEL: in bit;
        Z: out bit);
end MUX2;

```

Multiplexer: descrizione dataflow


```

architecture DATA_FLOW1 of MUX2 is
begin
  Z <= A when (SEL = '0') else
    B ;
end DATA_FLOW1;

architecture DATA_FLOW2 of MUX2 is
begin
  Z <= (A and not SEL) or (B and SEL);
end DATA_FLOW2;

```

Multiplexer a 4 vie

 

SEL0	SEL1	A	B	C	D	Z
0	0	0	—	—	—	0
0	0	1	—	—	—	1
0	1	—	0	—	—	0
0	1	—	1	—	—	1
1	0	—	—	0	—	0
1	0	—	—	1	—	1
1	1	—	—	—	0	0
1	1	—	—	—	1	1

```

entity MUX4 is
  port (A, B, C, D, SEL0, SEL1: in bit;
        Z: out bit);
end MUX4;

```

Multiplexer a 4 vie: dataflow

```

architecture DATA_FLOW1 of MUX4 is
begin
  Z <= A when (SEL0 = '0' and SEL1 = '0') else
    B when (SEL0 = '0' and SEL1 = '1') else
    C when (SEL0 = '1' and SEL1 = '0') else
    D;
end DATA_FLOW1;


architecture DATA_FLOW2 of MUX4 is
begin
  Z <= (A and not SEL0 and not SEL1)
    or (B and not SEL0 and SEL1)
    or (C and SEL0 and not SEL1) or (D and SEL0 and SEL1);
end DATA_FLOW2;

```

Stefano Ferrari ★ Università degli Studi di Milano

Architetture e reti logiche – VHDL ◇ Componenti combinatori in VHDL ◇ a.a. 2008/09 - p. 11/19

Multiplexer 4: descrizione strutturale

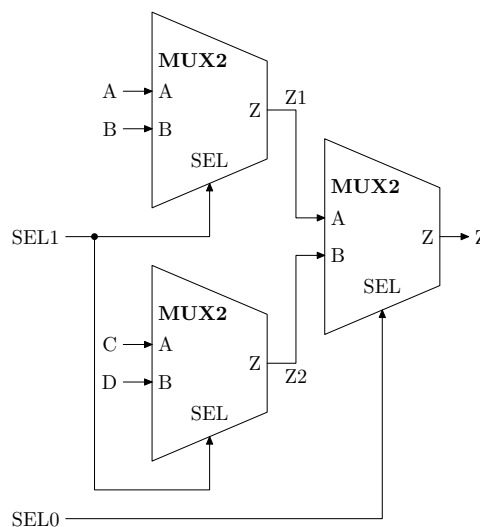

Stefano Ferrari ★ Università degli Studi di Milano

Architetture e reti logiche – VHDL ◇ Componenti combinatori in VHDL ◇ a.a. 2008/09 - p. 12/19


Multiplexer 4: descrizione strutturale (2)

```

architecture STRUCT2 of MUX4 is
  component MUX2
    port (A, B, SEL: in bit;
          Z: out bit);
  end component;
  signal Z1, Z2: bit ;
begin
  u1: MUX2 port map (A, B, SEL1, Z1);
  u2: MUX2 port map (C, D, SEL1, Z2);
  u3: MUX2 port map (Z1, Z2, SEL0, Z);
end STRUCT2;

```

Full adder

 

A	B	cin	S	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

```

entity fulladd is
  port (A, B : in bit;      -- addendi
        cin : in bit;     -- riporto in input
        S   : out bit;    -- somma (output)
        cout : out bit); -- riporto in output
end fulladd;

```


Full adder: descrizione dataflow

```

architecture dataflow of fulladd is
begin
    S <= A xor B xor cin;
    cout <= (A and B) or (A and cin) or (B and cin);
end dataflow;

```

Full adder a n bit

 


```

entity fulladd is
    port (A, B : in bit_vector(2 downto 0); -- addendi
          cin : in bit; -- riporto in input
          S : out bit_vector(2 downto 0); -- somma
          cout : out bit); -- riporto in output
end fulladd;

```


Full adder a 3 bit: modello strutturale

 

Stefano Ferrari ★ Università degli Studi di Milano

Architetture e reti logiche – VHDL ◊ Componenti combinatori in VHDL ◊ a.a. 2008/09 - p. 17/19

Full adder a 3 bit: modello strutturale (2)

```

architecture struct of fulladd3 is
  component fulladd
    port (A, B : in std_logic;
          cin : in std_logic;
          S   : out std_logic;
          cout : out std_logic);
  end component;

  signal t : std_logic_vector(0 to 3);

begin

```

(continua)

Stefano Ferrari ★ Università degli Studi di Milano

Architetture e reti logiche – VHDL ◊ Componenti combinatori in VHDL ◊ a.a. 2008/09 - p. 18/19

Full adder a 3 bit: modello strutturale (3)

(continua)

```
begin  
  t(0) <= cin;  
  u0: fulladd port map (A(0), B(0), t(0), S(0), t(1));  
  u1: fulladd port map (A(1), B(1), t(1), S(1), t(2));  
  u2: fulladd port map (A(2), B(2), t(2), S(2), t(3));  
  cout <= t(3);  
end struct;
```